

AIM:

To design and implement the two bit half adder using Logisim simulator.

PROCEDURE:

- 1) Pick and place the necessary gates.
- 2) Insert 2 inputs into the canvas.
- 3) Connect the inputs to the XOR gate and AND gate.
- 4) Insert 2 outputs into the canvas.
- 5) Make the connections using the connecting wires.
- 6) Verify the truth table.

TRUTH TABLE:**A****B****S****C**

0
0
0
0


0
1
1
0

1
0
1
0

1
1
0
1

S = A XOR B C = A AND B

OUTPUT

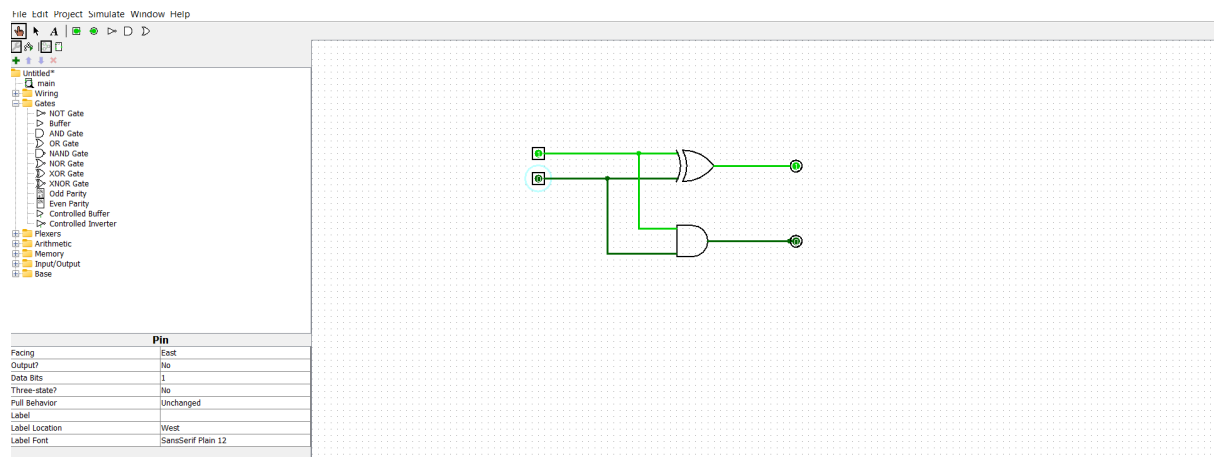

RESULT:

Thus

2-bit half adder has been designed and implemented successfully using logisim simulator.